

Lab 2: Scale

Tuesday, February 23, 2021 4:21 PM



Safari

Lab 3: Measuring mass using a strain gauge

Goal: Measure mass using a special voltage divider, an amplifier and a strain gauge.

Learning objectives

- Combine voltage dividers in parallel ("*Wheatstone bridge*") to measure a small ΔV ;
- Use a strain gauge to sense small changes in length caused by a force;
- Operate a potentiometer to balance a *Wheatstone bridge*;
- Use an instrumentation amplifier and explain its effect;
- Construct a calibration curve for your scale;
- Determine the sensitivity of your scale;

Visual Summary

1
meet the strain gauge




2
build & test circuit



4
calibrate scale



3
add amplification

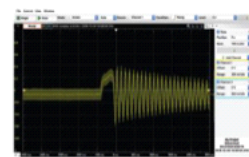

5
plot & analyze data



6
create & submit report




In this lab, you will make measurements of mechanical strain in small aluminum beams as you bend them. We will also work with our first integrated circuit component on the breadboard, the instrumentation amplifier.

1. Meet the strain gauge

The strain gauge is nothing more than a resistor whose value changes when it is elongated or compressed. When elongated, the small wires which make up the strain gauge get longer and thinner and the resistance goes up. When compressed the wires get shorter and fatter and the resistance goes down. When a strain gauge is stretched, its resistance changes according to the following formula

$$\frac{\Delta R}{R} = G_F \frac{\Delta L}{L}$$

where G_F is the gauge factor (it is 2.1 for our sensors), R is the starting resistance of the strain gauge (120 Ω in our case), ΔR is the change in resistance, ΔL is the local change in the length of the material, and L is the initial un-stretched length. The ratio of lengths is known as the mechanical strain. Since strain is usually quite small, the change in resistance is also quite small. Strain is a normalized measure of how much the material deforms.

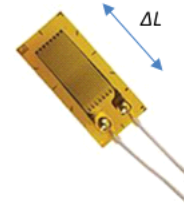

2. Build & test circuit

The classic circuit for measuring resistance change is the Wheatstone bridge, shown below in Figure 1 (left). At first glance, this may look like a strange circuit, but it is simply two voltage dividers wired so they are in parallel with one another.

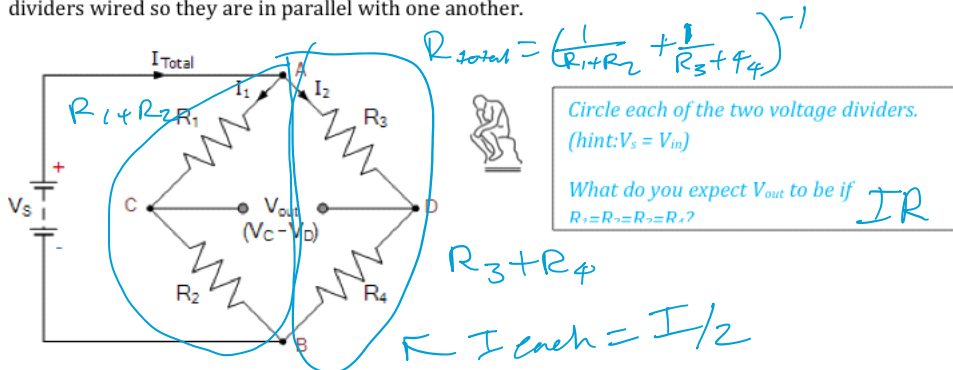


Figure 1. Wheatstone bridge. Image source: <https://www.electronics-tutorials.ws/blog/wheatstone-bridge.html>

We've redrawn the Wheatstone bridge in Figure 2, below, with our strain gauge as one of the resistors. In our case, the nominal resistance of the strain gauge is 120 Ω when no load is applied. If all the resistances are exactly 120.0 Ω , the bridge is balanced.

If all components had the exact resistances as shown in Figure 2, at the midpoint between the resistors on the left and right branch, the voltage would be 2.5V relative to ground on each side. Thus, when you measure the difference, ΔV_{meas} , you would see 0V at no mechanical load on the strain gauge. If the resistance of the strain sensor then changes, you would measure a slight voltage difference across ΔV_{meas} which is related to the resistance change of the strain gauge.


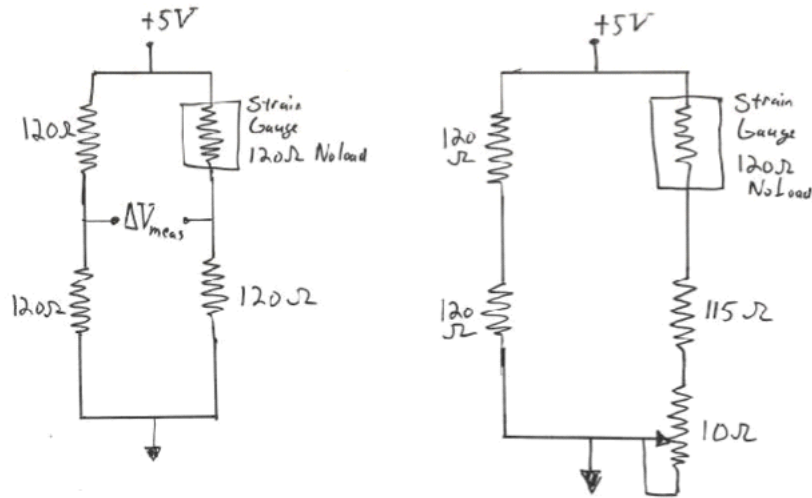
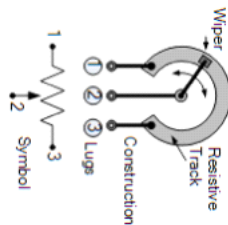


Figure 2: Classic Wheatstone bridge for sensing small changes in resistance. On the left is a classic bridge with perfectly matched resistors. On the right, we use a potentiometer to balance the bridge such that the measured voltage is 0 when the strain gauge is unloaded. This accounts for the fact that the resistors are not precise.

Unfortunately, real resistors come with finite tolerances (e.g., $\pm 1\%$ for most of the resistors we use). Consequently, we typically add a variable resistor (a trim potentiometer or "pot") to the bridge, as shown in Figure 2 (right), in order to balance it manually.

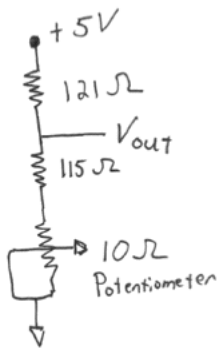You may recognize this potentiometer configuration from Class 4.



Schematic: <https://www.electronics-tutorials.ws/resistor/potentiometer.html>

We will balance the bridge by adjusting the potentiometer and measuring ΔV_{meas} .



How will we know that the bridge is balanced?




w/No strain, $\Delta V_{meas} = 0$

We will start by building the basic circuit shown in Figure 3. Just to make your life confusing there are two types of strain gauges – the type doesn't matter but the connection is slightly different for the two types.


Sorry. We bought different parts on accident and didn't notice until time was too short to reorder.

Some strain gauges we have are 3-wire measurements to reduce error due to resistance of the wire leads.

The 2-wire gauges are simple resistors

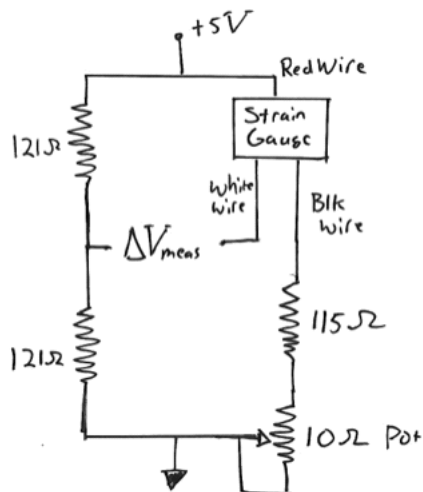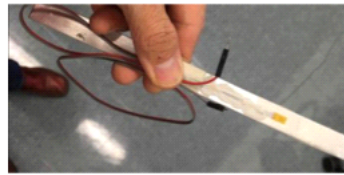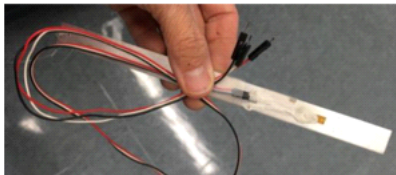

Three Wire Strain Gauge

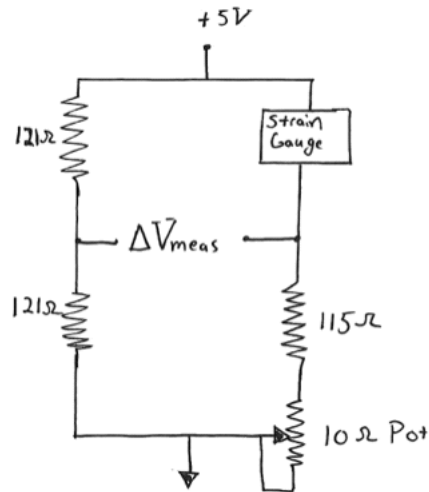

Two Wire Strain Gauge

Figure 3. The first circuit you should build to measure strain via the change in resistance.

The nominal resistor values are not always those we would like to use (e.g., the closest standard value for 1% resistors to 120Ω is 121Ω). We use resistors that are $\pm 1\%$ of their nominal value.




It turns out that if we substitute any two resistors of equal resistance in the left leg of the Wheatstone bridge (i.e., one of the voltage dividers), the circuit will still function the same.*


Why?

Because they'd still split the voltage equally

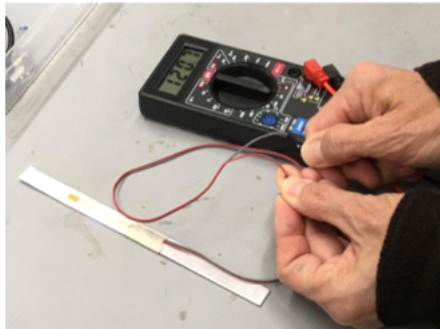**The resistors must also have a tolerance of $\pm 1\%$.*



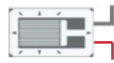Before wiring the strain gauges, make sure that it has a resistance of $\sim 120\Omega$.




For the 3-wire gauges, measure the resistance from the red to each of the other leads.



If is the $R \ll 120\Omega$ or $R \gg 120\Omega$, the strain gauge is probably broken.

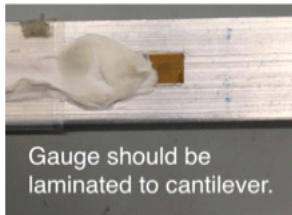If so, please inform an instructor & get a different assembly.




Check your strain gauge for mechanical integrity.

If the gauge is delaminated, please inform an instructor & get a different assembly.

Connect the Analog Discovery

Use either Ch1 or Ch2 to measure the ΔV across the two mid-points of each voltage divider (Fig 3, $\Delta V_{\text{measure}}$).

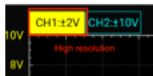The ΔV should be ~ 0 . Zoom in the y-axis scale on the Scope to 50 mV per division. Adjust the potentiometer up and down. You should be able to control the voltage difference across the bridge to be around ± 5 -20 mV. *You will need the high resolution setting (bottom right in scope pullout) for Ch1*



(Upper left on scope: High resolution should show $\pm .2V$)



If you are unable to make the voltage change by twisting the potentiometer – something is wrong. If you are unable to push the voltage difference both above and below zero – the system won't work.

TROUBLESHOOTING TIPS



System not working as expected? What exactly is happening?

e.g: You turn the potentiometer across its full range and it looks like $\Delta V \sim 0$.

These are your assumptions so far. You can test any of them.

Wavegen connected & measuring properly

Power supply plugged in, supplying +5V & 2.5V

Elements are wired properly in the circuit;

Components (R's) are correct values;

Scope screen is sufficient resolution (~ 50 mV/div)

Once you are sure the circuit is working, balance the bridge and set the measured voltage to zero as best you can. It is not crucial that it is perfectly zero, in fact it is likely to jump a little when you take the screwdriver off the potentiometer.

Test with the cantilever/strain gauge

Zoom your scope axis to be around 10 mV/division.

Clamp the beam to cantilever off your desk where the strain gauge is **facing up and is just over the edge of the desk**.

Push the beam downward, **gently**; you should notice changes on the order of a few mV.



If you do not see changes \sim mV, do **not push harder.**

The aluminum beam will easily deform.

3. Add amplification

The $\Delta V_{\text{measured}}$ from the Wheatstone bridge resulting from a change in the strain gauge's resistance is \sim mV; we can amplify it for a better measurement. To perform the amplification, we will use the instrumentation amplifier "AD623".

We will discuss in lab how it works. In short, we will use this chip as a "black box" that takes a voltage difference and amplifies it by a large number on your breadboard.



Build the circuit shown in Figure 4 (with slight modification if you are doing the two-wire measurement). Note the schematic uses a capacitor with a value of 100 picofarads (pF). We have not discussed capacitors yet (next week). The capacitor helps remove radio frequency noise, but does not influence the basic operation of the circuit. Once you have the circuit built, you will need to hook up the scope again. Plug channel 1 positive input into the output of the instrumentation amplifier and the negative input for channel 1 into the 2.5 V reference on your breadboard.


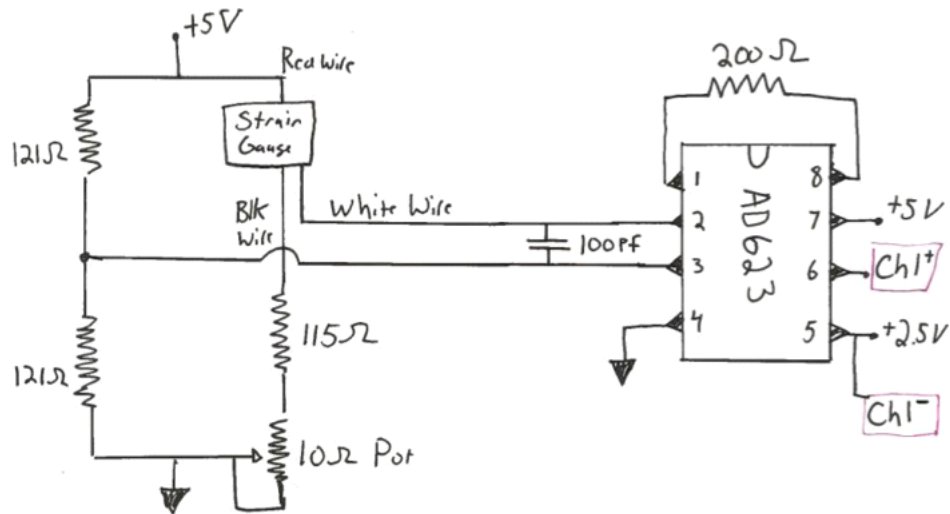


Figure 4: Final strain gauge circuit.

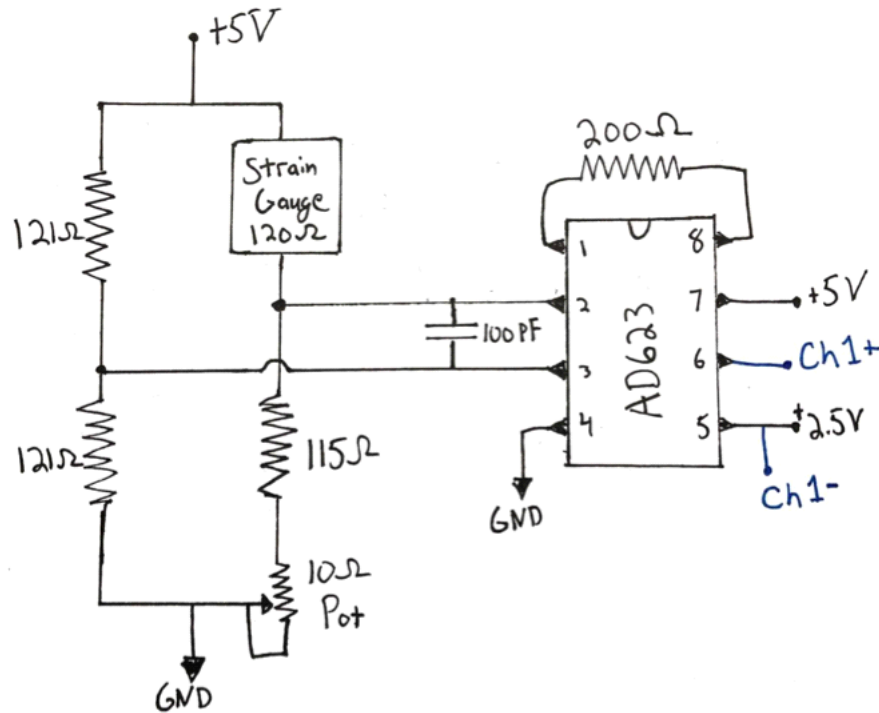

Rebalance the bridge to zero (or close as you can get).

The output of the instrumentation amplifier is designed to be,

$$V_{out} = V_{ref} + G(V_+ - V_-)$$

In the above expression V_{out} is the voltage on pin 6, V_+ is the voltage on pin 3, V_- is the voltage on pin 2, and V_{ref} is the voltage on pin 5. Note that V_{ref} is set to 2.5V in our experiment. When we measure V_{out} relative to V_{ref} , we can measure the change in voltage caused by the beam being bent up or down.



What is the expected V_{out} when the beam is at rest (i.e., no strain on the gauge)?

V_{ref}

The value of G , the gain, is set by the expression:

$$G = 1 + \frac{100,000 \, \Omega}{R_G}$$

The gain is selected by the user (i.e. you) by selecting the value of the resistor connecting pins 1 and 8. We use a 200 Ohm resistor, therefore $G=501$ for our circuit. Note that the above equation is determined by the internal design of the chip and is not some fundamental law of physics (though later in the course we could understand where the design equation comes from!).

Once the system is balanced, try pushing down slightly on the end of the beam with your finger and you should see a nice voltage change. You will need to adjust the scope scale back to something like 1V/division. Push the beam up and it should change in the other direction. Flick it and you should see damped oscillations. When you unload the beam, the signal should return to zero. Note that it is probably impossible to perfectly balance things with the potentiometer. This is fine. It is really only the change that is important anyway.

4. Calibrate the scale

Now you're going to create a calibration curve by measuring the voltage output by taking the voltage reading for 1, 2 and 3 washers, all of known mass (they are marked with their mass in grams).

Note that you may need to balance the bridge by adjusting the potentiometer so that you have close to zero volts with no load.

You might see some oscillations as the system comes to rest. If the washer is swinging, the signal will show an oscillation at the frequency of the swing. If this is the behavior you observe, then everything is working great.



Do not add more than 300 grams.

W 50.7359 mV + 6.806



This final plot with your best fit calibration curve should be part of your lab report. This calibration line becomes your scale.



ΔV is linear with ΔR_{gauge} ; ΔR_{gauge} is linear with strain; Strain of the gauge is linear with mass.

How do you expect the ΔV to vary with mass?

Linear

Is the shape of your calibration curve as you expect?

Test your calibration curve by measuring the mass of a different washer. Measure the voltage output. You can now **compute the mass from the calibration**. Compute the %error for your strain



gauge scale, $\%error = \left| \frac{x_{\text{measured}} - x_{\text{known}}}{x_{\text{known}}} \right|$

Test: 51 mV @ 57.1g

5. Plot and analyze

In your lab report, **discuss your scale sensitivity** (A measure of sensitivity is $\frac{dV_{\text{output}}}{dm_{\text{ass}_{\text{input}}}$.)

For your circuit, a 20 mV change in the output voltage seems to be easily discernable. For a 20 mV change,

- What is the associated change in electrical resistance of the strain gauge? You will need to do a little analysis here.
- What is the mass that was applied to the scale to get this change of 20 mV on the output voltage?



6. Create and submit report

| mV | g |
|----|------|
| 4 | 0 |
| 9 | 14 |
| 30 | 27.7 |
| 45 | 40.7 |



ISIM Lab 2: An Analysis of Strain Sensors for Weight Measurement on the Surface of the Earth

Ari Porad

March 2, 2021

Abstract

A strain sensor attached to an aluminium bar was used to measure the weight of several washers. Several measurements were used to calibrate the voltage-weight relationship of the scale ($n=3$). Another measurement was then used to test the accuracy of the generated calibration curve ($n=1$). We found this scale to be a relatively accurate for measuring the weight of small objects (less than 60g), with an error of 4.67% for our test object (who's true weight was 57.1g).

1 Methodology

1.1 Strain Sensor Setup

Measuring the weight (and therefore mass) of objects is a common problem that billions of people face each day. Consequently, cheap, simple, and reliable methods of weighing objects are highly desirable.

We aimed to evaluate the use of an electric strain gauge to measure the weight of an object. The strain gauge was laminated to an aluminium bar, which was clamped to the edge of a table, as shown in Figure 1. Weights¹ could then be hung from the aluminum bar (centered on the black line). This would cause the aluminum to strain and deform, therefore altering the resistance of the strain gauge.



Figure 1: For this experiment, a strain gauge was laminated to an aluminum bar, then clamped to the edge of a table.

¹For the purposes of this experiment, we used single washers of varying sizes as our test weights.

1.2 Electronics

In order to accurately measure small changes in the resistance of the strain gauge, we used a Wheatstone bridge, amplified using an AD623 IC and balanced using a 10Ω potentiometer (see Figure 2). An O-Scope was used to measure the voltage across the strain sensor from within the bridge (see Figure 3).

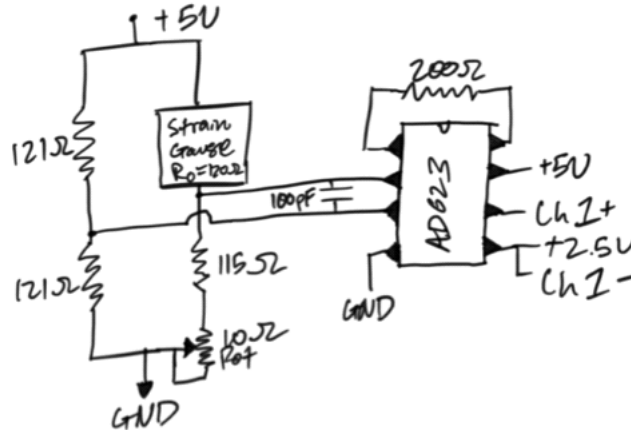


Figure 2: We connected the strain gauge to an amplified Wheatstone bridge.

1.3 Calibration

We knew that a strain sensor has a linear relationship between strain and resistance, which itself has a linear relationship to voltage. Additionally, an aluminum bar has a linear relationship between force applied (due to gravity) and strain. Consequently, we knew that there would be a linear relationship between the weight of an object hanging from the aluminum bar and the resistance of the strain gauge.

We determined this relationship by weighing three calibration objects, each with a known (but different) weight. For each object, we allowed the voltage reading to settle and then recorded the voltage measured by the O-Scope.

Finally, we computed a linear regression between measured voltage and known weight. This regression allowed us to calculate the measured weight from an arbitrary voltage across the strain sensor.

1.4 Testing

As the last step in our experiment, we weighed a fourth object of known weight, which had not yet been weighed by our strain gauge scale. We used the calculated linear regression to determine the measured weight of the object, and compared that to known weight to calculate the error.

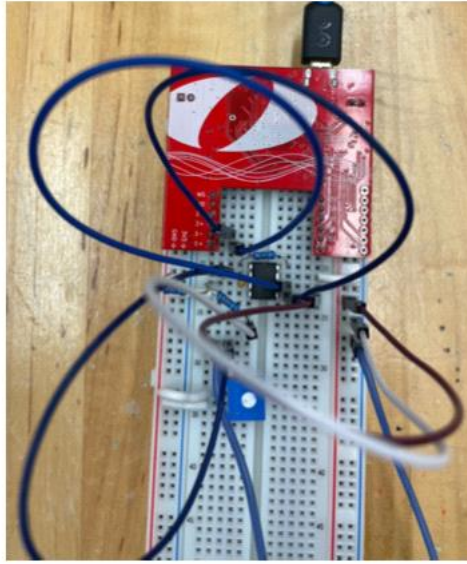


Figure 3: Our breadboard, as used to measure the voltage across the strain gauge using an amplified Wheatstone bridge.

2 Results

2.1 Calibration

We calibrated our scale using three objects, with the following known weights and measured voltages:

| Measured Voltage (mV) | Known Weight (g) |
|-----------------------|------------------|
| 9mV | 14g |
| 30mV | 27.7g |
| 45mV | 40.7g |

Table 1: Measured voltages and known weights of our three calibration objects.

From this data, we calculated the following linear regression, which represents our scale's relationship between voltage (V) and mass (m). A visual comparison between our data and the regression can also be seen in Figure 4.

$$m = 1.35V - 9.0792 \quad (1)$$

2.2 Testing

After calculating our trendline, we weighed another test object, measured the voltage across the strain gauge, and calculated the measured weight of the object. The object's true weight was 57.1g

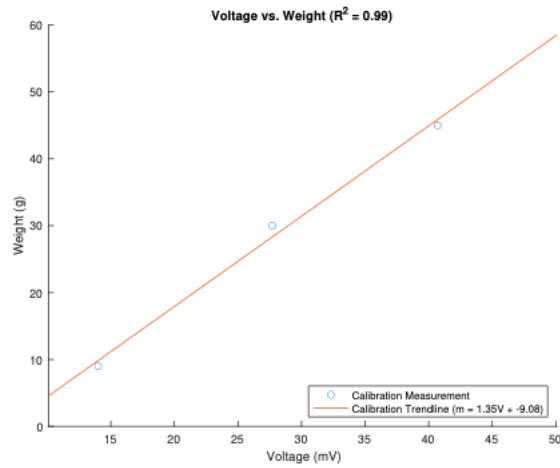


Figure 4: Voltage vs. weight, showing our three calibration weights and our calculated calibration trendline. $R^2 = 0.99$

while its measured weight was 59.77g (see Figure 5) for an error of 4.67%. That error is fairly low, making our strain gauge a decent means of weight measurement.

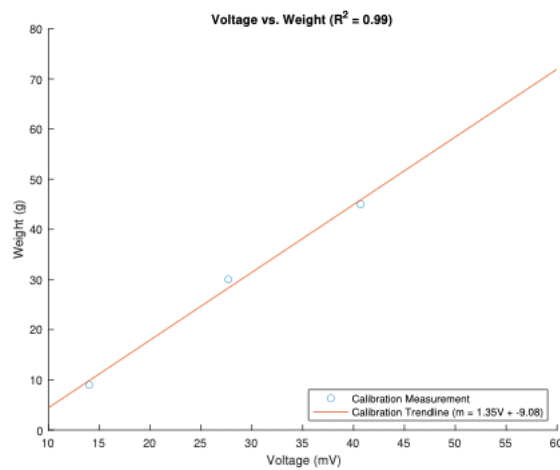


Figure 5: Voltage vs. weight, showing the test object's measured and true weight in addition to our three calibration weights and our calculated calibration trendline.

2.3 Sensitivity

The sensitivity of our strain gauge was $0.74 \frac{mV}{g}$. Assuming that a $5mV$ change is easily detectable by our equipment, the resolution of our scale is $6.76g$, which is a reasonable level of precision for many tasks.

For our system, a $20mV$ change in output voltage represents an additional $27.03g$ of weight added to the scale, as calculated by our linear regression. It also corresponds to a 1.48Ω change in the electrical resistance of the strain gauge, as calculated from the formulae given by the ISIM teaching team for voltage dividers, the strain gauge resistance/deformation relationship, and the AD632 input/output relationship.

3 Finishing Remarks

This experiment demonstrated that an electric strain gauge has significant potential a mechanism for measuring weight. More experimentation is required to determine how to reduce noise and increase precision.