

PS9

By Ari Porad

Introduction to Sensors, Instrumentation, and Measurement

Note

As specified by the assignment instructions, the resistors and capacitors have the following values for all circuits:

$$R_1 = 1k\Omega$$

$$R_2 = 10k\Omega$$


$$C_1 = 1\mu F (10^{-6} F)$$

$$C_2 = 0.1\mu F (10^{-7} F)$$

Circuit 1: RC + OpAmp

$$V_{-1} =$$


$$-\frac{1}{C_1 w} \left(R_1 - \frac{1}{C_1 w} \right)$$

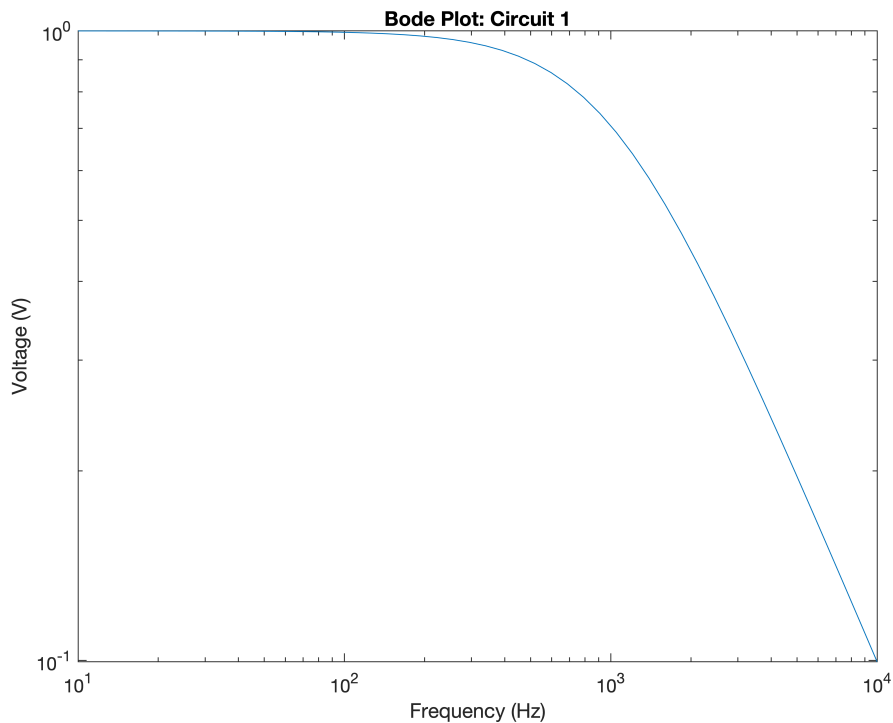

Circuit 2: R + (R || C) + OpAmp

$$V_{-2} =$$


$$\frac{1}{\left(\frac{1}{R_2} + 1 C_2 w i\right)} \left(R_1 + \frac{1}{\frac{1}{R_2} + 1 C_2 w i} \right)$$

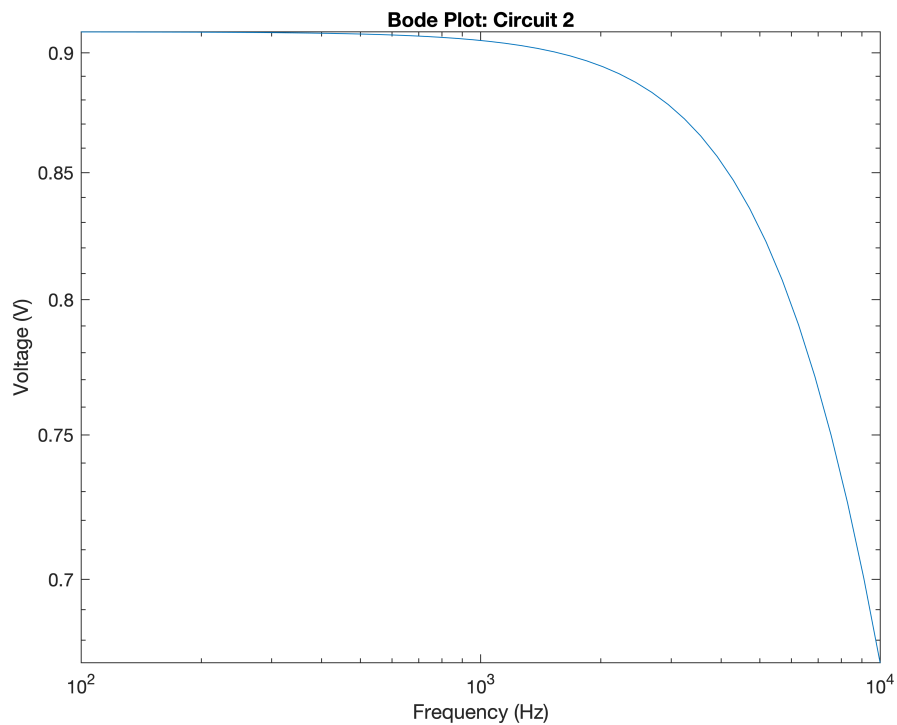

Circuit 3: CR + OpAmp

V₃ =


$$\frac{1 C_1 R_1 w i}{1 + 1 C_1 R_1 w i}$$

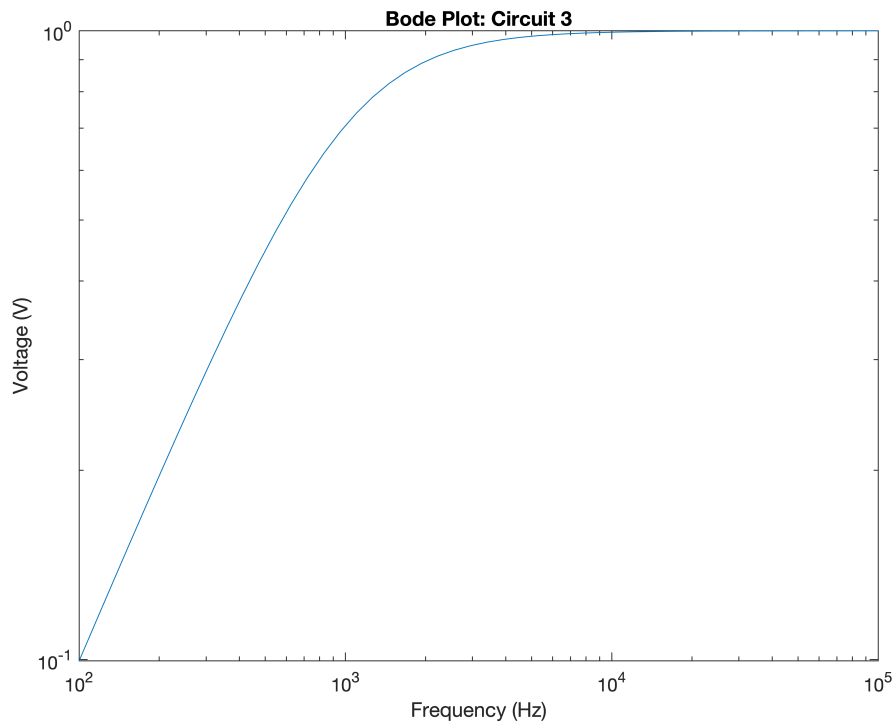

Circuit 4: R + C + (C || R) + OpAmp

V₄ =


$$\frac{1}{\left(\frac{1}{R_2} + 1 C_2 w i\right) \left(R_1 + \frac{1}{\frac{1}{R_2} + 1 C_2 w i} - \frac{1 i}{C_1 w}\right)}$$

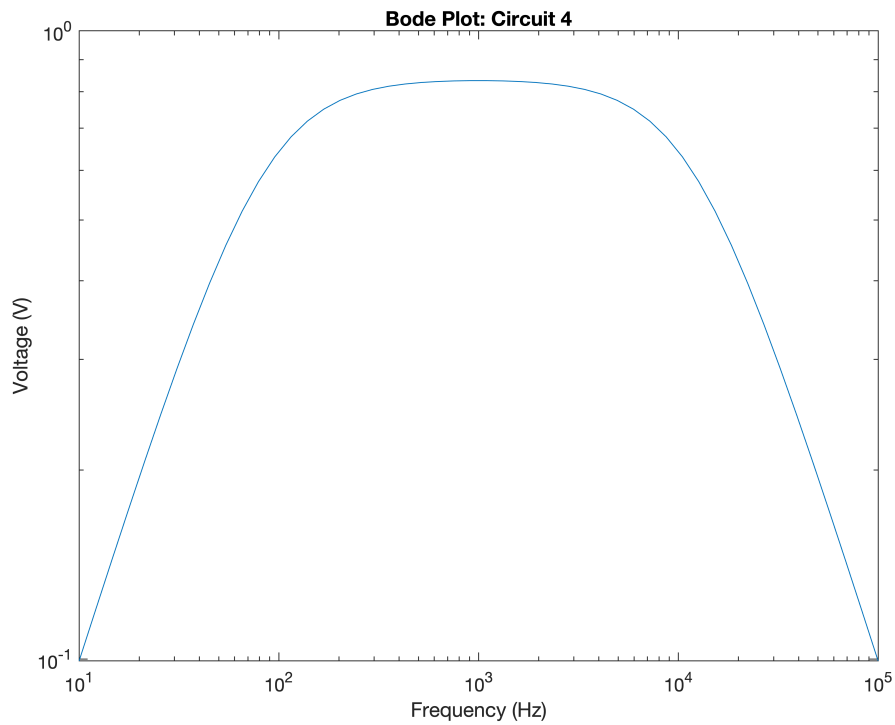

Circuit 5: RC Voltage Divider

V₅ =


$$\frac{1}{1 + j\omega C_1 R_1}$$

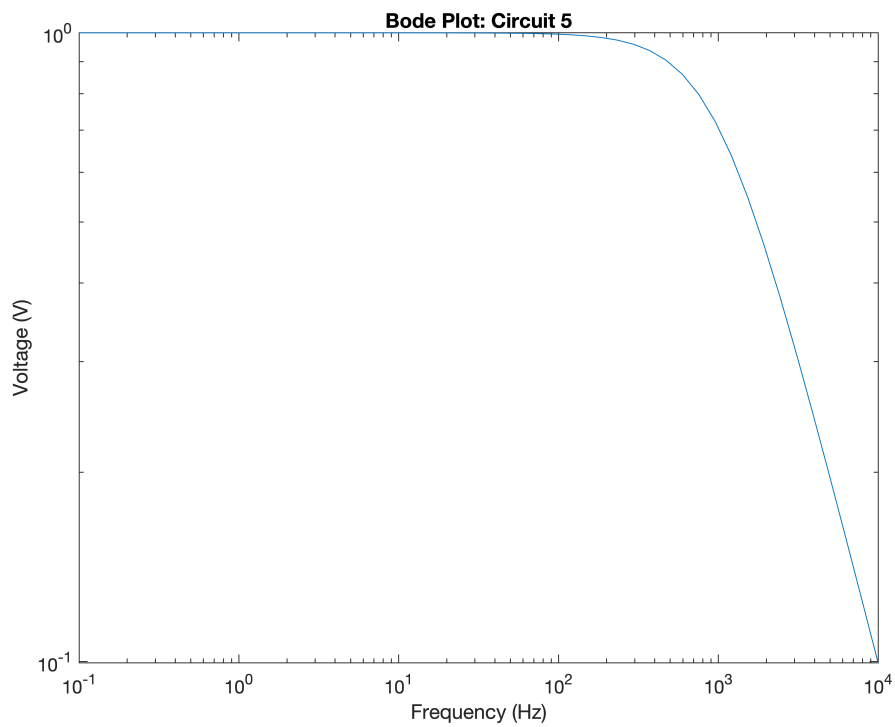

Circuit 6: RC + RC

$V_6 =$


$$\frac{1}{(1 + j\omega C_1 R_1)(1 + j\omega C_2 R_2)}$$

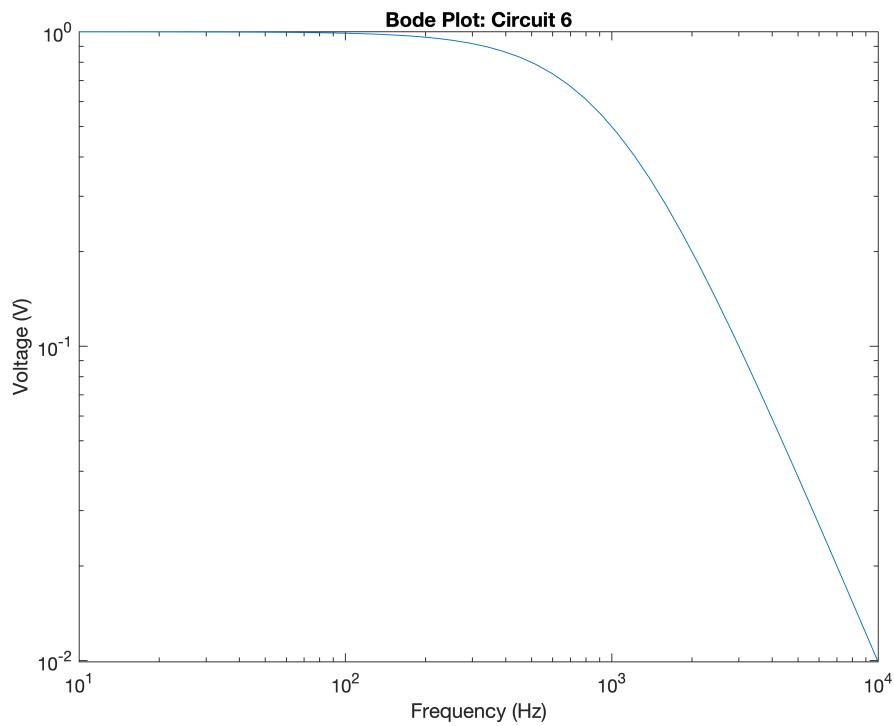

Circuit 7: RC + RC but reversed

$V_7 =$

$$\frac{1}{(1 + j\omega C_1 R_1)(1 + j\omega C_2 R_2)}$$

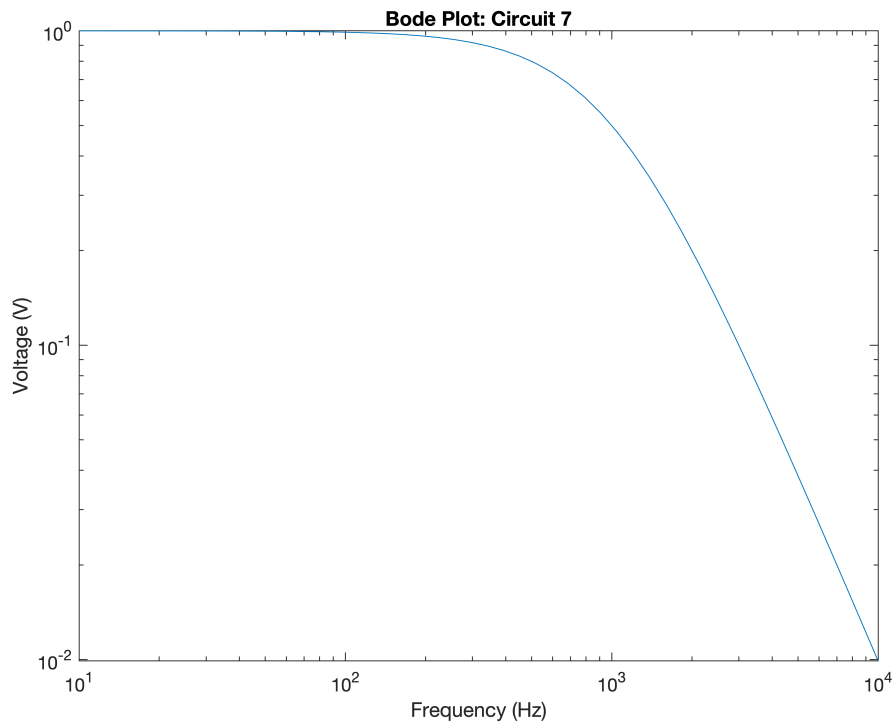

Circuit 8: RC + CR

$V_8 =$

$$\frac{1 C_1 R_1 w i}{(1 + 1 C_1 R_1 w i) (1 + 1 C_2 R_2 w i)}$$

