

PS9: Complex Filters

Thursday, April 22, 2021 5:16 PM



PSet9-Complex Filters

Problem set

Analysis of filters with complex impedance

For each of the circuits in the table, figure out the complex number that represents the ratio of the output voltage divided by the input voltage. Write your final result in the tables. For each circuit in the table, create a plot of the magnitude of this complex number as a function of frequency. Put both the magnitude and frequency on a logscale. For each circuit use:






- $R_1 = 1 \text{ k}\Omega$ $C_1 = 1 \mu\text{F}$
- $R_2 = 10 \text{ k}\Omega$ $C_2 = 0.1 \mu\text{F}$

Remember, the impedance of a resistor and capacitor are

- $Z_R = R$
- $Z_C = \frac{1}{j\omega C}$

	$\frac{V_{out}}{V_{in}} = \frac{\left(\frac{1}{j\omega C_1}\right)}{R_1 + \frac{1}{j\omega C_1}}$ $= \frac{1}{j\omega C_1(R_1 + \frac{1}{j\omega C_1})}$ $= \frac{1}{j\omega C_1 R_1 + 1}$
	$\frac{V_{out}}{V_{in}} = \frac{1/(1/R_2 + j\omega C_2)}{R_1 + 1/(1/R_2 + j\omega C_2)}$ $= \frac{1/(1/R_2 + j\omega C_2)}{R_1 + 1/(1/R_2 + j\omega C_2)}$ $= \frac{R_1}{1/R_2 + j\omega C_2 R_2} + \frac{1}{R_1 + 1/(1/R_2 + j\omega C_2)}$
<p>CR Filter</p>	$\frac{V_{out}}{V_{in}} = \frac{j\omega R_1 C_1}{1 + j\omega R_1 C_1}$

$$Z_2 = \frac{1}{\frac{1}{R_2} + j\omega C_2}$$

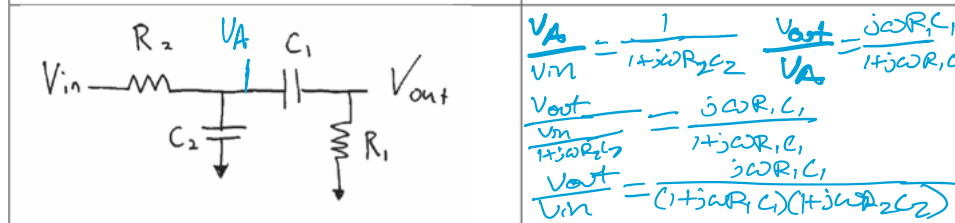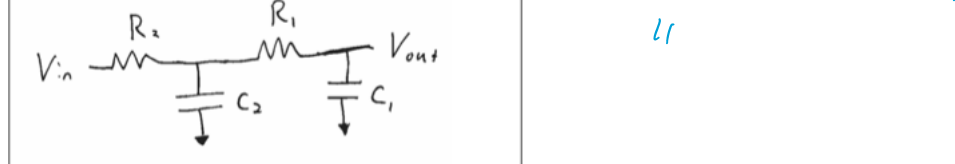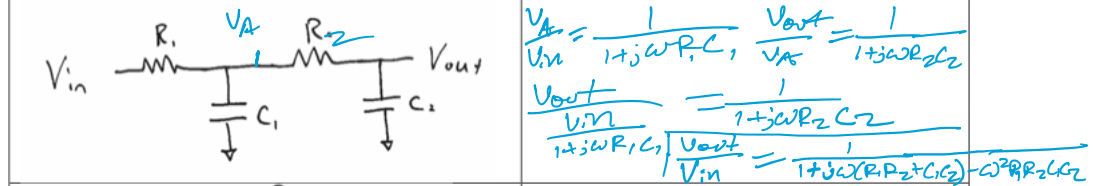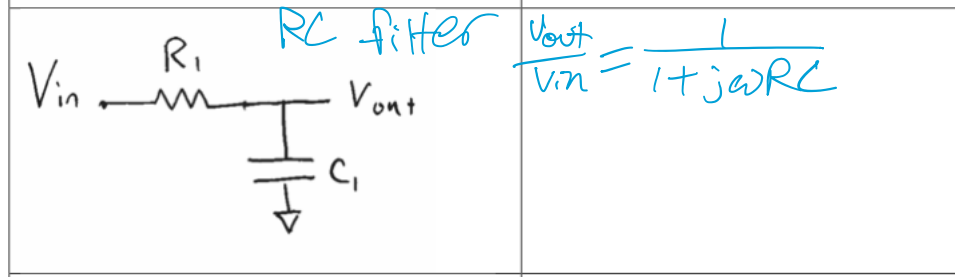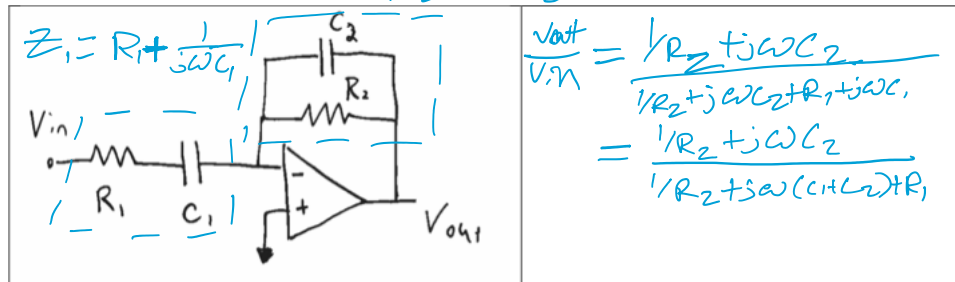

PS9

By Ari Porad

Introduction to Sensors, Instrumentation, and Measurement

Note

As specified by the assignment instructions, the resistors and capacitors have the following values for all circuits:

$$R_1 = 1k\Omega$$

$$R_2 = 10k\Omega$$


$$C_1 = 1\mu F \ (10^{-6} F)$$

$$C_2 = 0.1\mu F \ (10^{-7} F)$$

Circuit 1: RC + OpAmp

$$V_1 =$$


$$-\frac{1}{C_1 w} \left(R_1 - \frac{1}{C_1 w} \right)$$

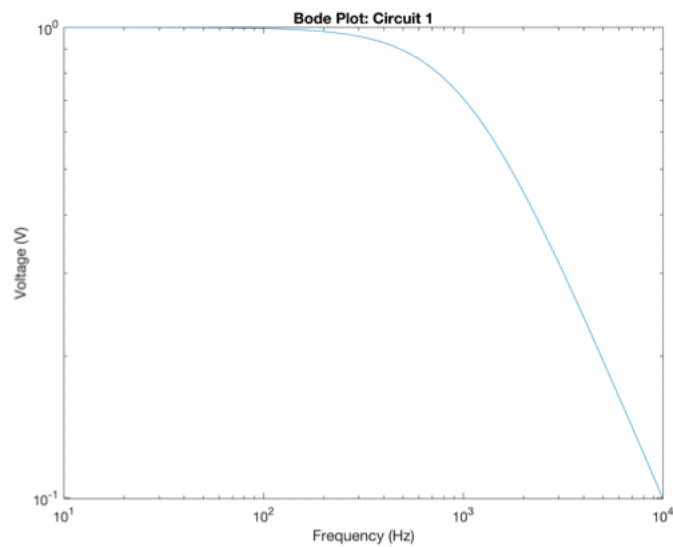

Circuit 2: R + (R || C) + OpAmp


$$V_2 =$$

$$\frac{1}{\left(\frac{1}{R_2} + 1 C_2 w i\right)} \left(R_1 + \frac{1}{\frac{1}{R_2} + 1 C_2 w i}\right)$$

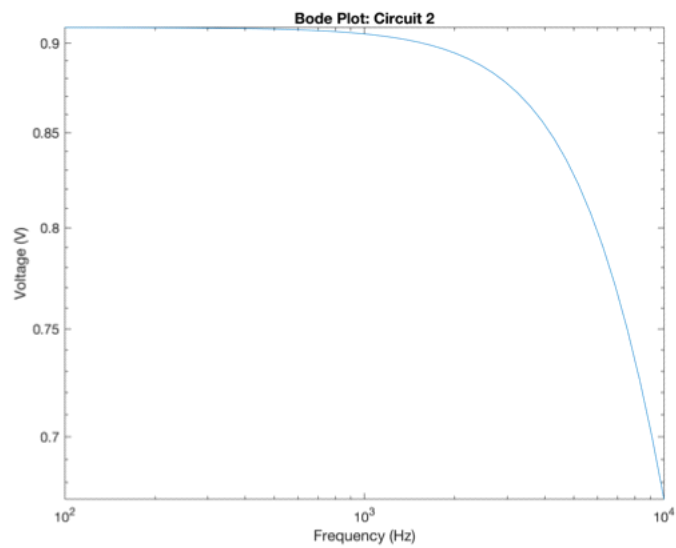

Circuit 3: CR + OpAmp


$$V_3 = \frac{1 C_1 R_1 w i}{1 + 1 C_1 R_1 w i}$$

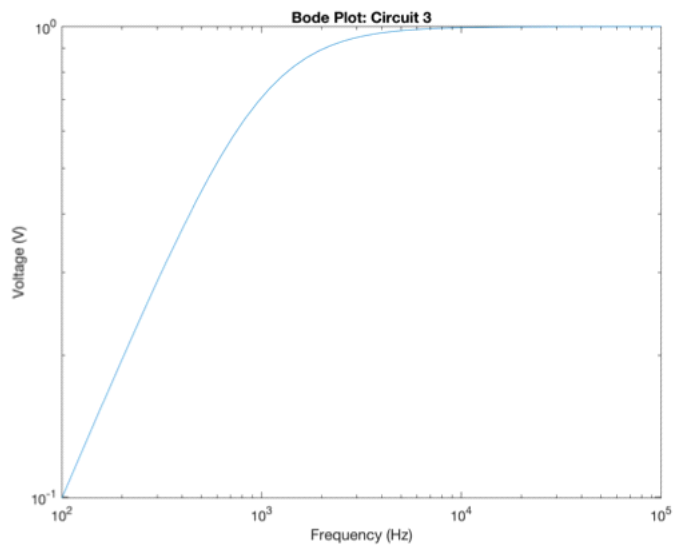

Circuit 4: R + C + (C || R) + OpAmp


$V_4 =$

$$\frac{1}{\left(\frac{1}{R_2} + 1 C_2 w i\right) \left(R_1 + \frac{1}{\frac{1}{R_2} + 1 C_2 w i} - \frac{1 i}{C_1 w}\right)}$$

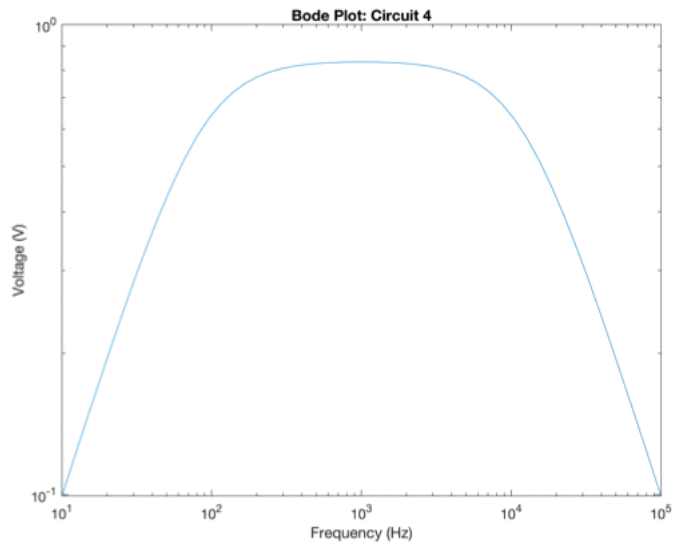

Circuit 5: RC Voltage Divider


$$V_5 = \frac{1}{1 + j\omega R_1 C_1}$$

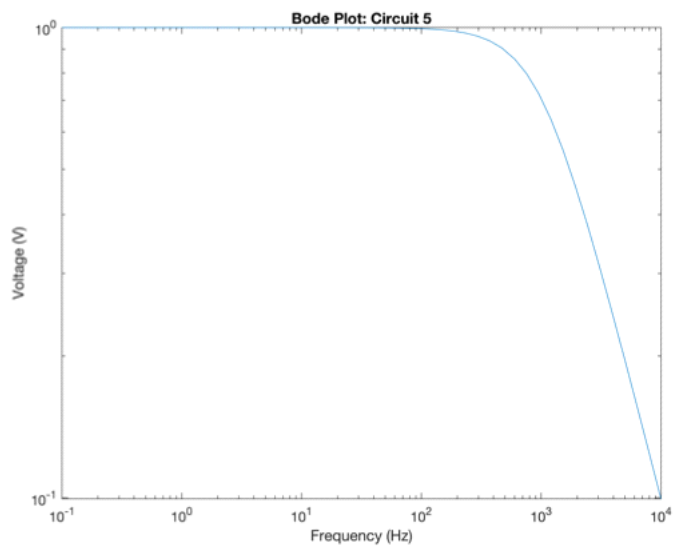

Circuit 6: RC + RC

V₆ =


$$\frac{1}{(1 + j\omega C_1 R_1)(1 + j\omega C_2 R_2)}$$

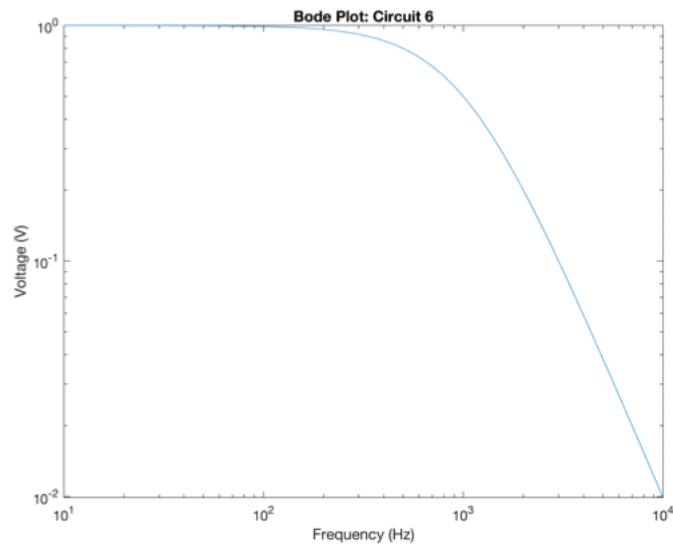

Circuit 7: RC + RC but reversed

V₇ =

$$\frac{1}{(1 + j\omega C_1 R_1)(1 + j\omega C_2 R_2)}$$

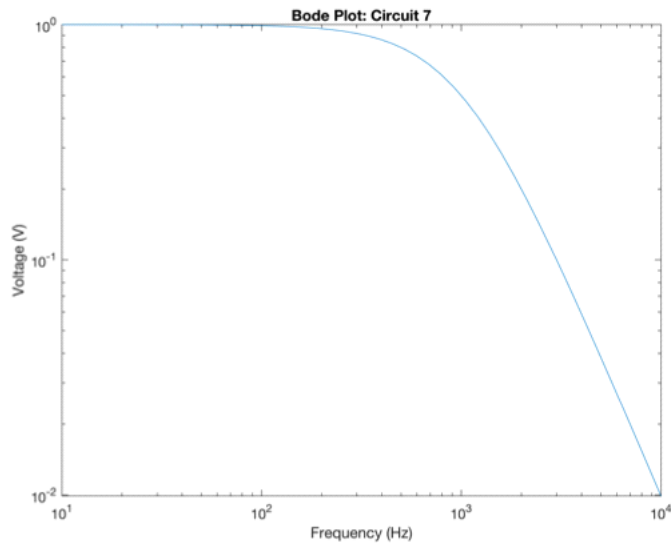

Circuit 8: RC + CR

$V_8 =$

$$\frac{1 C_1 R_1 w i}{(1 + 1 C_1 R_1 w i) (1 + 1 C_2 R_2 w i)}$$

